

CE 1911

Single Cycle Processor III

Simple Data Path

- Arithmetic and logical

$\text{fn Reg1, Reg2, Wreg} \quad \text{Wreg} \leftarrow \text{Reg1 fn Reg2}$

- Memory

ld Reg1, Wreg

$\text{Wreg} \leftarrow \text{MEM}(\text{Reg1})$

st Reg1, Reg2

$\text{MEM}(\text{Reg1}) \leftarrow \text{Reg2}$

- Immediate

$\text{ld Reg1, "imm value"} \quad \text{Reg1} \leftarrow \text{"imm value"}$

Simple Data Path


- Arithmetic and logical

sub RA, RB, RC

$$RC \leftarrow RA - RB$$

Instruction				Reg 1		Reg 2		W Reg		Immediate Value					
0	1	0	1	0	0	0	1	1	0	0	0	0	0	0	0

or	0000
and	0001
nor	0010
nand	0011
add	0100
sub	0101
slt	0110
ld	1000
st	1001
ldi	1100

 

00 – A
01 – B
10 – C
11 – D


Technically these are don't care but we will always code them as 0s

Simple Data Path

sub RA, RB, RC

- Operation
- Arithmetic and Logical

Instruction				Reg 1		Reg 2		W Reg		Immediate Value					
0	1	0	1	0	0	0	1	1	0	0	0	0	0	0	0

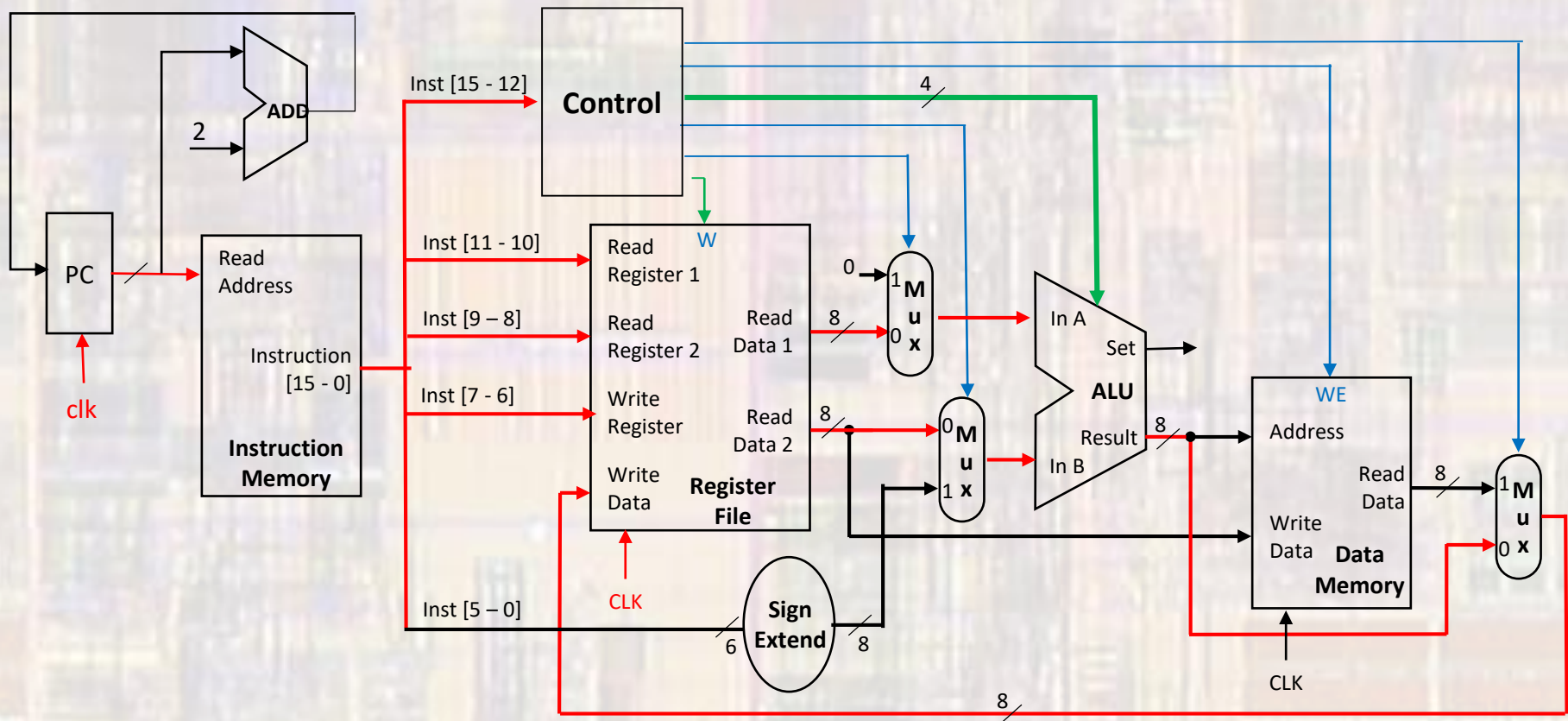

Simple Data Path

- Instruction Format

- Instruction Encoding

- LD

$WRreg \leftarrow MEM(Reg1)$

- LD RA, RC

$RC \leftarrow MEM(RA)$

Instruction				Reg 1		Reg 2		WR Reg		Immediate Value					
1	0	0	0	0	0	x	x	1	0	0	0	0	0	0	0

or ↑ 0000
 and ↑ 0001
 nor ↑ 0010
 nand ↑ 0011
 add ↑ 0100
 sub ↑ 0101
 slt ↑ 0110
 ld ↑ 1000
 st ↑ 1001
 ldi ↑ 1100

RA ↑ RC
 ↑ ↗
 00 – A
 01 – B
 10 – C
 11 – D

↑
 added to Reg 1 to
 make the memory
 address


Simple Data Path

- Operation

- LD

LD RA, RC

Instruction				Reg 1		Reg 2		WR Reg		Immediate Value							
1	0	0	0	0	0	x	x	1	0	0	0	0	0	0	0	0	0

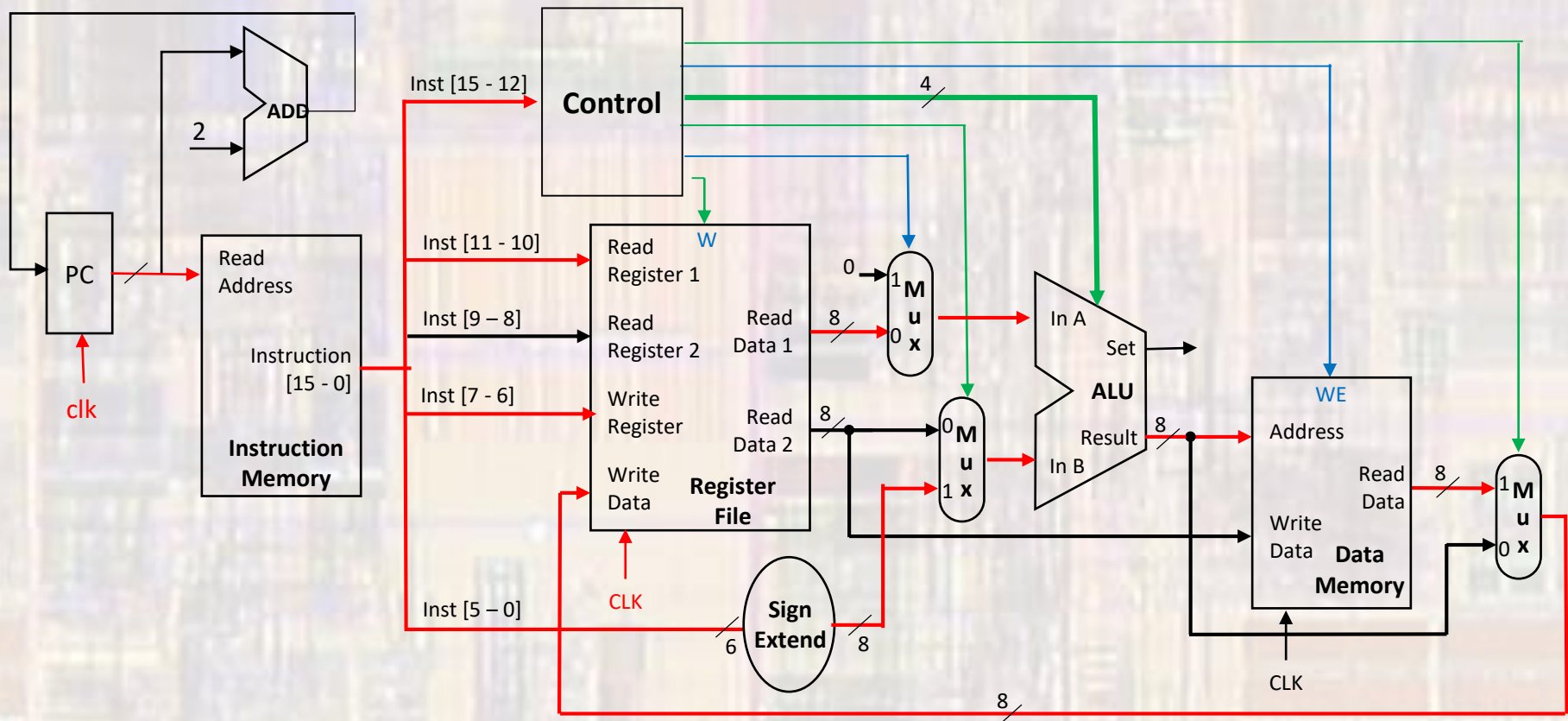

Simple Data Path

- Instruction Format

- Instruction Encoding

- ST Reg1, Reg2

$\text{MEM}(\text{Reg1}) \leftarrow \text{Reg2}$

- ST RA, RC

$\text{MEM}(\text{RA}) \leftarrow \text{RC}$

Instruction				Reg 1		Reg 2		WR Reg		Immediate Value					
1	0	0	1	0	0	1	0	x	x	0	0	0	0	0	0

or ↑ 0000
 and ↑ 0001
 nor ↑ 0010
 nand ↑ 0011
 add ↑ 0100
 sub ↑ 0101
 slt ↑ 0110
 ld ↑ 1000
 st ↑ 1001
 ldi ↑ 1100

RA ↑ RC
 ↑ ↑
 00 – A
 01 – B
 10 – C
 11 – D

↑
 added with Reg 1 to
 make the memory
 address


Simple Data Path

- Operation

- ST

ST RA, RC

Instruction				Reg 1		Reg 2		WR Reg		Immediate Value					
1	0	0	1	0	0	1	0	x	x	0	0	0	0	0	0

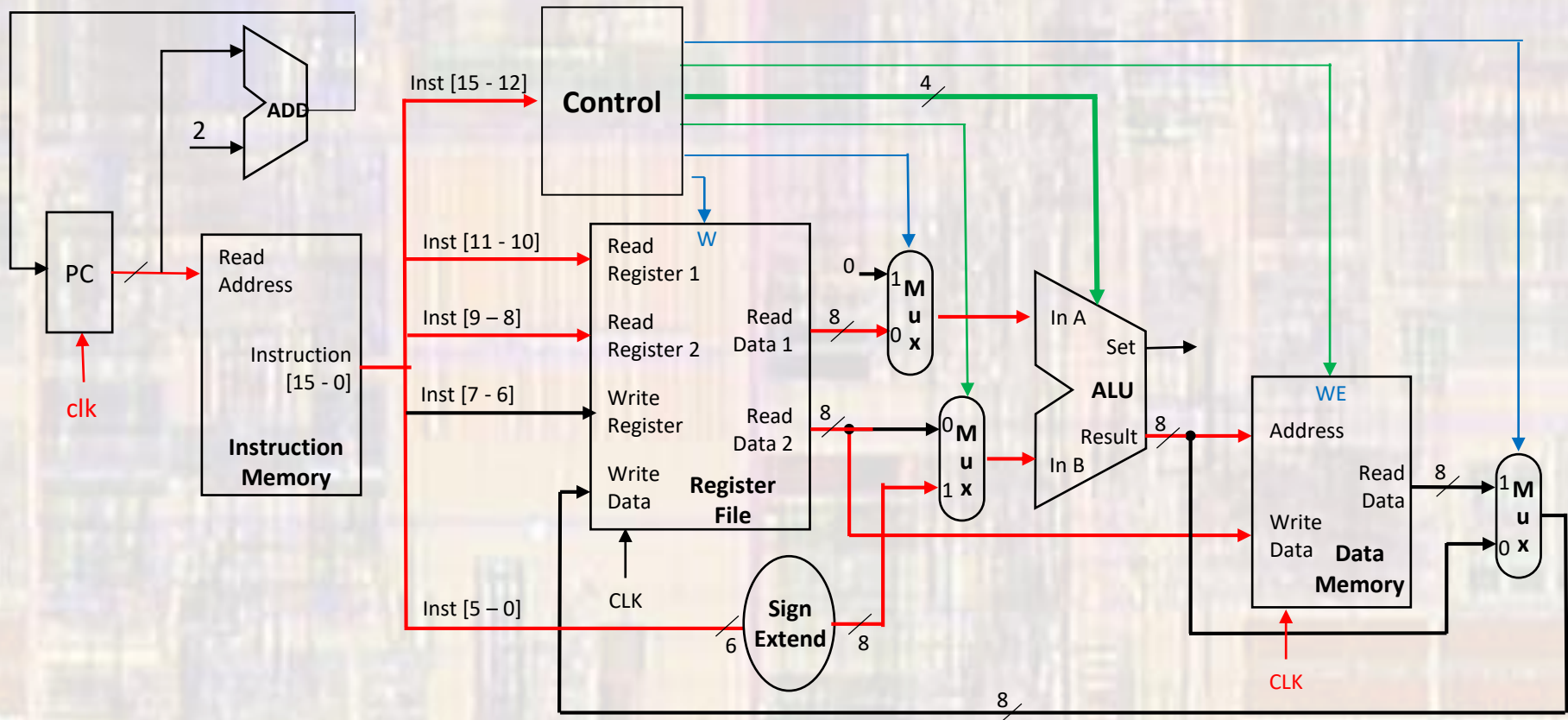

Simple Data Path

- Instruction Format

- Instruction Encoding

- LDI

WrReg \leftarrow Imm extended

- LDI RA, 0x12

RA \leftarrow 0x12

Instruction				Reg 1		Reg 2		WR Reg		Immediate Value					
1	1	0	0	x	x	x	x	0	0	0	1	0	0	1	0

or ↑ 0000
 and ↑ 0001
 nor 0010
 nand 0011
 add 0100
 sub 0101
 slt 0110
 ld 1000
 st 1001
 ldi 1100

↙ ↑ ↘
 RA
 00 – A
 01 – B
 10 – C
 11 – D

↑
 signed Hex
 0x20 to 0x1F


 100000 to 011111
 -32 to 31

Simple Data Path

- Operation
- LDI

LDI RA, 0x12

Instruction				Reg 1		Reg 2		WR Reg		Immediate Value					
1	1	0	0	x	x	x	x	0	0	0	1	0	0	1	0

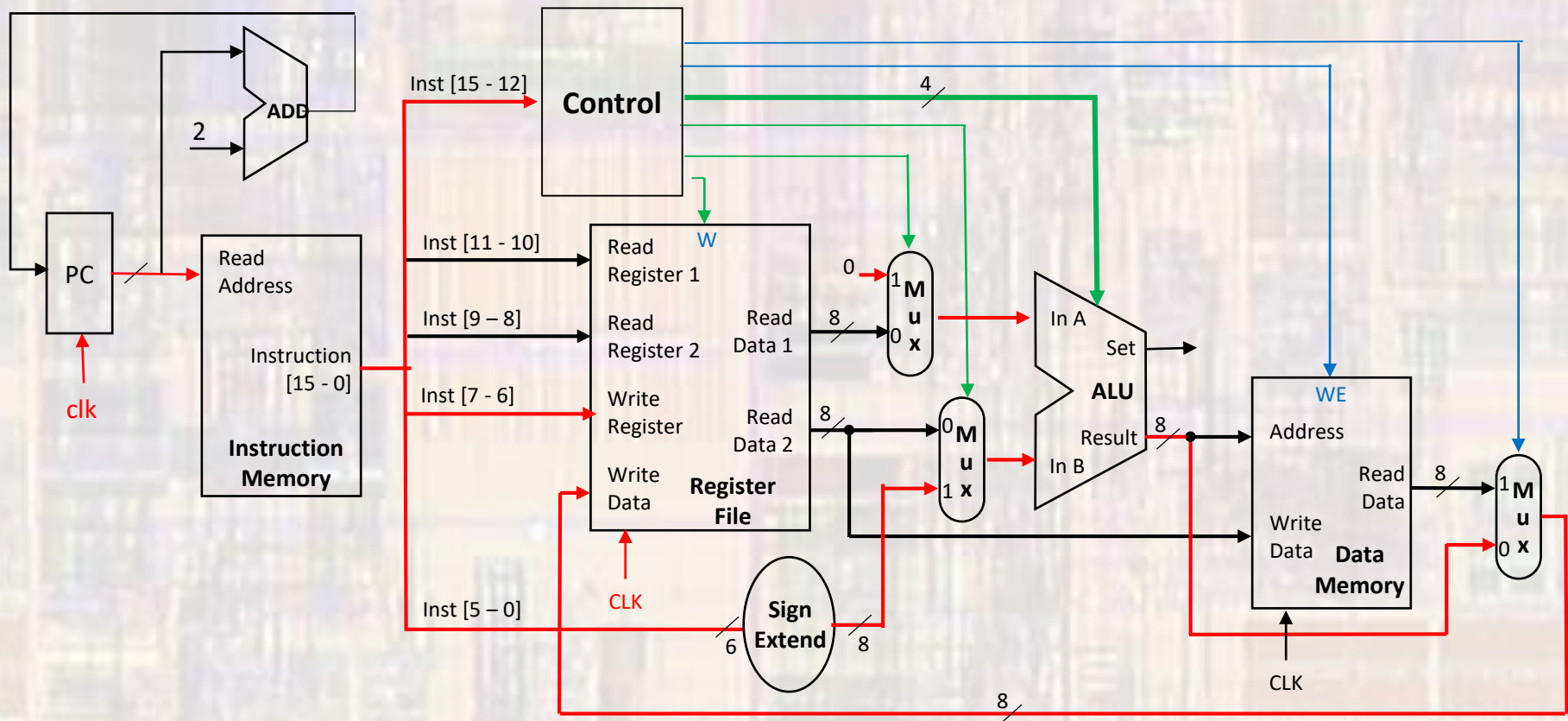

Simple Data Path

- ALU Control
- Basic ALU control mapping

Operation	invA	negB	ctl[1]	ctl[0]
AND	0	0	1	1
OR	0	0	1	0
NOR	1	1	1	1
NAND	1	1	1	0
ADD	0	0	0	1
SUB	0	1	0	1
SLT	0	1	0	0

Simple Data Path


- ALU Control
- Full ALU control mapping

Operation	invA	negB	ctl[1]	ctl[0]
AND	0	0	1	1
OR	0	0	1	0
NOR	1	1	1	1
NAND	1	1	1	0
ADD	0	0	0	1
SUB	0	1	0	1
SLT	0	1	0	0
LD	0	0	0	1
ST	0	0	0	1
LDI	0	0	0	1

adding 0 from instruction
adding 0 from instruction
adding 0 from mux

Simple Data Path

- Additional Control Signals

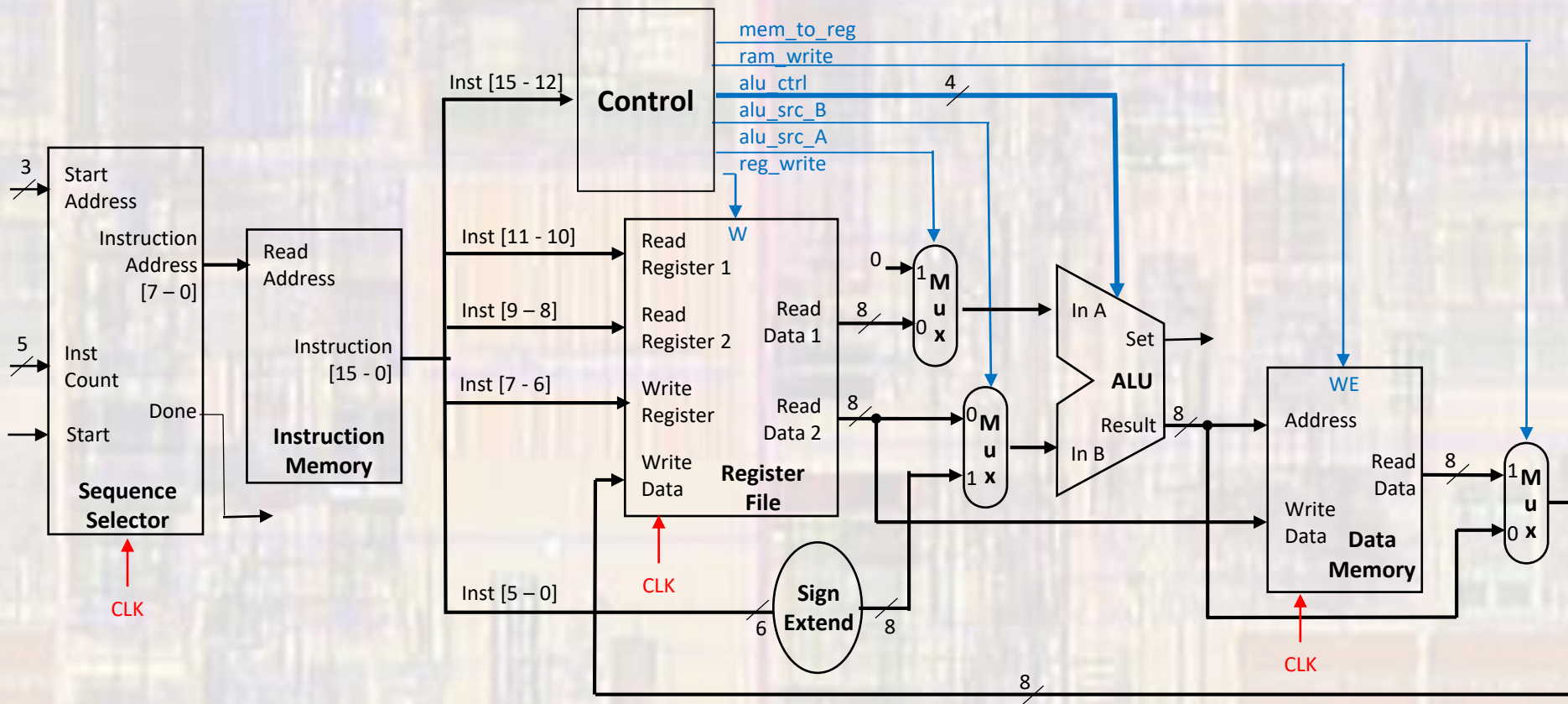

Simple Data Path

- Additional Control Signals
 - mem_to_reg
 - Selects between the ALU output and the RAM read data value to pass to the Write data input of the register file
 - “1” only on LD instructions
 - ram_write
 - Enable writing to the Data RAM
 - “1” only on ST instructions

Simple Data Path

- Additional Control Signals
 - alu_src_B
 - Selects between the Read data 2 output of the register file and the sign extended immediate signal to pass to ALU input B
 - “0” for arithmetic and logical instructions
 - “1” for LD, ST and LDI instructions
 - alu_src_A
 - Selects between the Read data 1 output of the register file and 0 to pass to ALU input A
 - “1” only on LDI commands

Simple Data Path

- Additional Control Signals
 - reg_write
 - Enable writing to the Register File
 - “0” only on ST instructions

Simple Data Path

- Performance Issues
 - Longest delay determines clock period
 - Critical path: load instruction
 - Instruction memory → register file → ALU → data memory → register file
 - Not feasible to vary period for different instructions
 - Violates design principle
 - Making the common case fast
 - We will improve performance by pipelining

Simple Data Path

- Assume RA, RB, RC, RD contain the values 0x11, 0x22, 0x44, 0x88 respectively

Provide the values for each signal after executing the instruction: `add RA, RB, RA` located in program memory at 0x56

Node	Value (hex)
A	0x58
B	0x4100
C	0x11
D	0x33
E	0x22
F	0x11
G	0x22
H	0x33
I	??
J	0x56

